

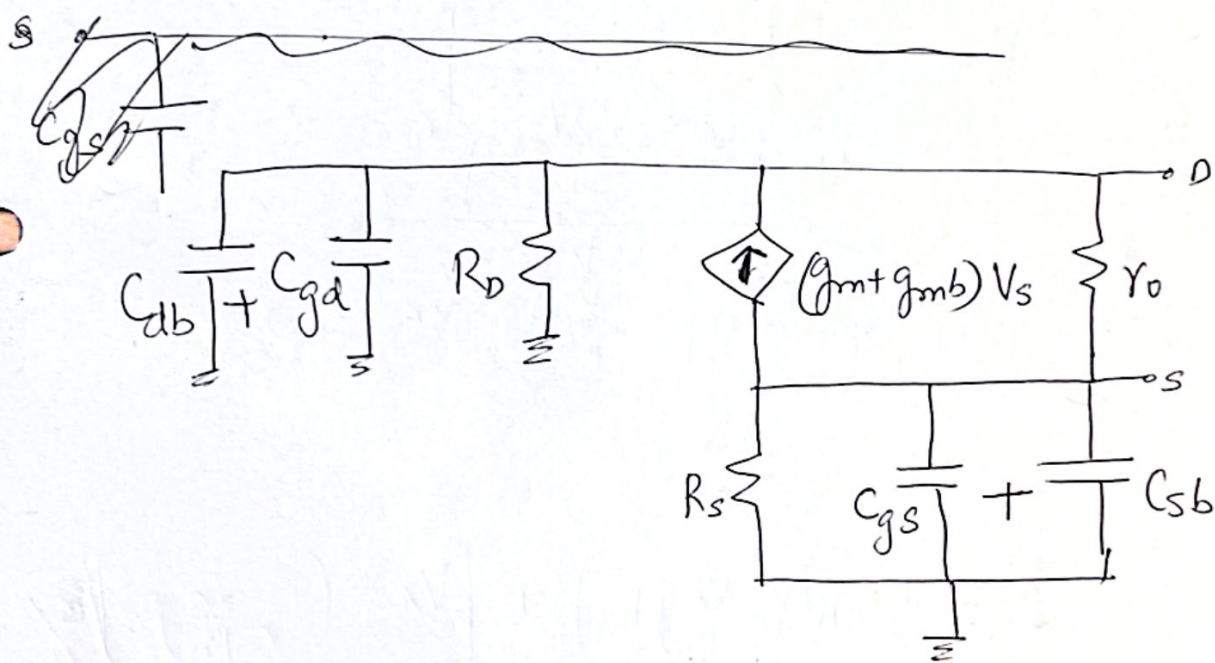
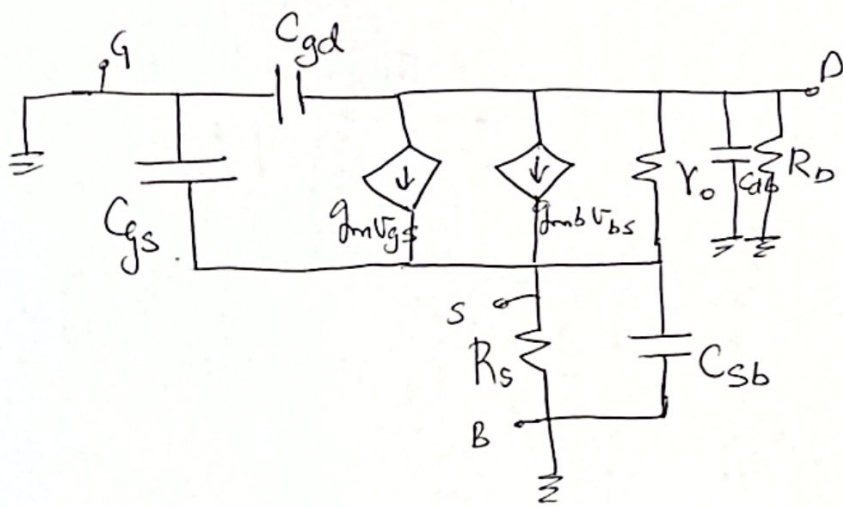


# Common Gate

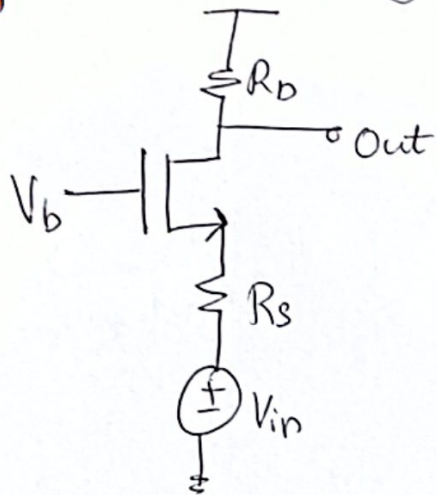

$C_{gs} + C_{sb}$  :

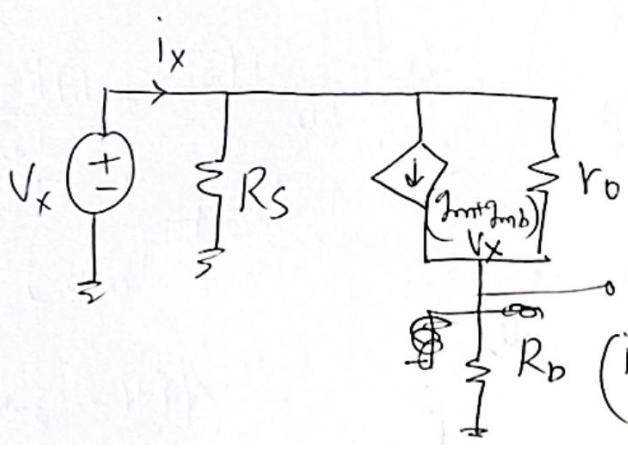


$$i_x = \frac{V_x}{R_s} + (g_m + g_{mb})V_x + \frac{(V_x - i_x R_s)}{r_o}$$

$$\Rightarrow V_x \left( g_{mt} g_{mb} + \frac{1+A}{R_S} \right) = i_x \left( 1 + \frac{R_D}{r_o} \right)$$

$$\Rightarrow R_S^0 = \frac{R_S \parallel Y_o \parallel \frac{1}{g_{mt} g_{mb}}}{1 + \frac{R_D}{r_o}} \approx R_S \parallel \frac{1}{g_{mt} + g_{mb}}$$

$C_{db} + C_{gd}$  :

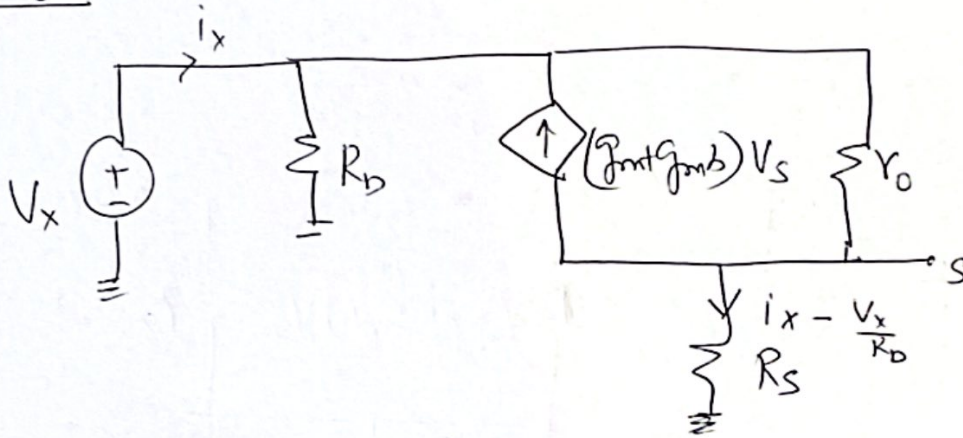

$$\Rightarrow i_x = \frac{V_x}{R_D} - (g_{mt} + g_{mb}) \left( i_x - \frac{V_x}{R_D} \right) R_S + \left[ V_x - \left( i_x - \frac{V_x}{R_D} \right) R_S \right] / Y_o$$

$$\Rightarrow i_x \left( 1 + (g_{mt} + g_{mb}) R_S + \frac{R_S}{r_o} \right) = V_x \left[ \frac{1}{R_D} + (g_{mt} + g_{mb}) \frac{R_S}{R_D} + \frac{1}{Y_o} + \frac{R_S}{R_D Y_o} \right]$$

$$\Rightarrow R_D^0 = \frac{\left[ \frac{1}{R_D} + (g_{mt} + g_{mb}) \frac{R_S}{R_D} + \frac{1}{Y_o} + \frac{R_S}{R_D Y_o} \right]}{\left[ 1 + (g_{mt} + g_{mb}) R_S + \frac{R_S}{r_o} \right]}$$

$$\Rightarrow R_b^0 = \frac{R_b \parallel R_b \left( \frac{R_s}{g_m + g_{mb}} \right) \parallel r_o \parallel \frac{r_o R_b}{R_s}}{1 + (g_m + g_{mb}) R_s + \frac{R_s}{r_o}}$$

$$\approx R_b$$

$$\Rightarrow \omega_{3dB} \approx \frac{1}{(C_{gs} + C_{sb}) \left( R_s \parallel \frac{1}{g_m + g_{mb}} \right) + (C_{gd} + C_{db}) (R_b)}$$

Again no Miller effect!




$$\approx \frac{1}{C_{gs} / g_m} \left( \frac{g_m}{C_{gs}} \right)$$

$$\omega_{3dB} \approx \frac{g_m}{C_{gs}} \frac{1}{R_b C_{gd} + \frac{C_{gs}}{g_m} \left( R_s \parallel \frac{1}{g_m} \right)}$$






# Summary

Gain of Common gate if  $R_{in} \neq 0$

$$a \frac{(g_m + g_{mb}) r_o R_D}{R_D + r_o + R_{in}((g_m + g_{mb}) r_o + 1)}$$

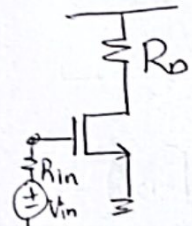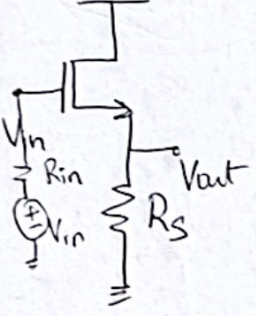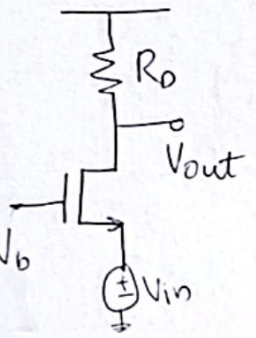Type	Low freq. Gain	Bandwidth	$R_{in}$	$R_{out}$
<p>Common Source</p> 	<p>(<del>Assuming</del>)  <math>-g_m (r_o \parallel R_D)</math>                      High                      Inverting</p>	$\frac{1}{R_{in} (1 + g_m R_D) C_{gd} + R_{in} C_{gs} + R_D C_{gd} + R_D C_{db}}$ Low (Miller)	$\infty$	$r_o \parallel R_D$
<p>Common Drain</p> 	<p><math>\frac{g_m (r_o \parallel R_S)}{1 + (g_m + g_{mb}) (r_o \parallel R_S)}</math>  <math>\approx 1</math>                      Noninverting</p>	$\frac{1}{R_{in} C_{gd} + \frac{C_{gs} + C_{sb}}{g_m + g_{mb}}}$ High (No Miller)	$\infty$	$R_S \parallel r_m \parallel r_{mb} \parallel r_o$ $\approx R_S \parallel r_m$
<p>Common Gate</p> 	<p>High                      Noninverting  <math>(g_m + g_{mb} + \frac{1}{r_o}) (r_o \parallel R_D)</math>  <math>\approx (g_m + g_{mb}) (r_o \parallel R_D)</math>                      Assuming <math>R_{in} = 0</math></p>	$\frac{1}{(C_{gs} + C_{sb}) (R_{in} \parallel \frac{1}{g_m + g_{mb}}) + (C_{gd} + C_{db}) R_D}$ $\approx \frac{1}{R_D C_{gd} + C_{gs} (R_S \parallel \frac{1}{g_m})}$ High (No Miller)	$r_m \parallel r_{mb} \parallel r_o$ $\approx r_m$	$r_o \parallel R_D$


# Cascode

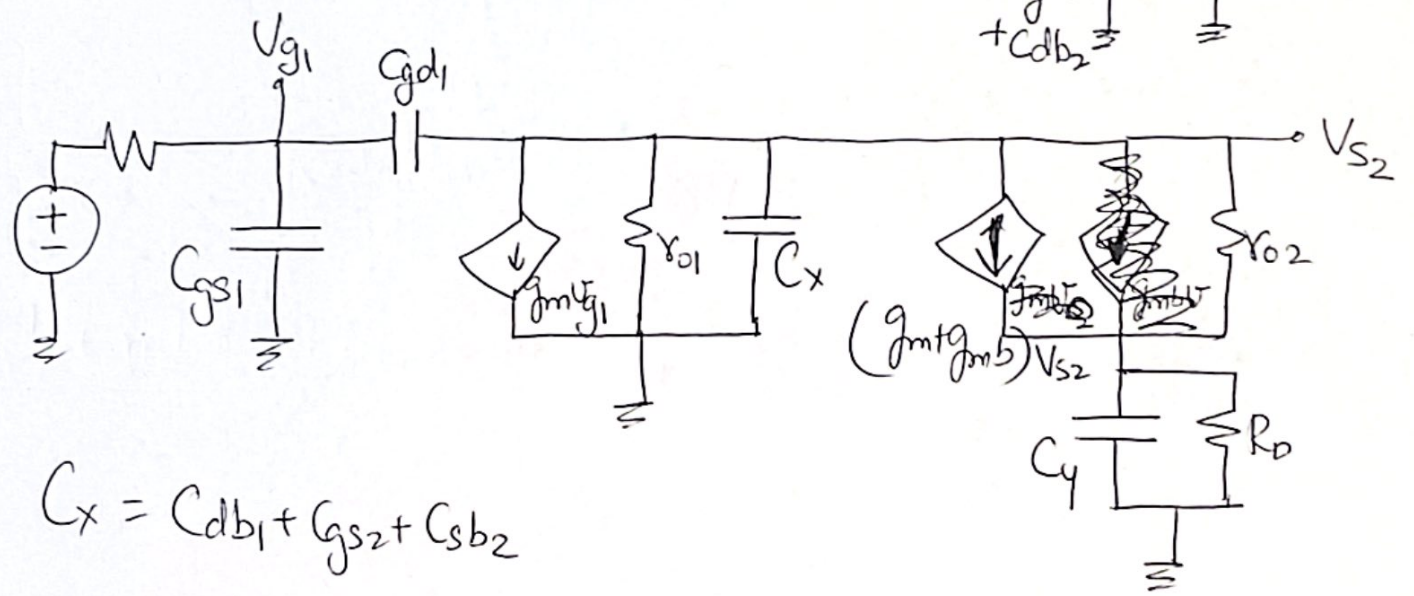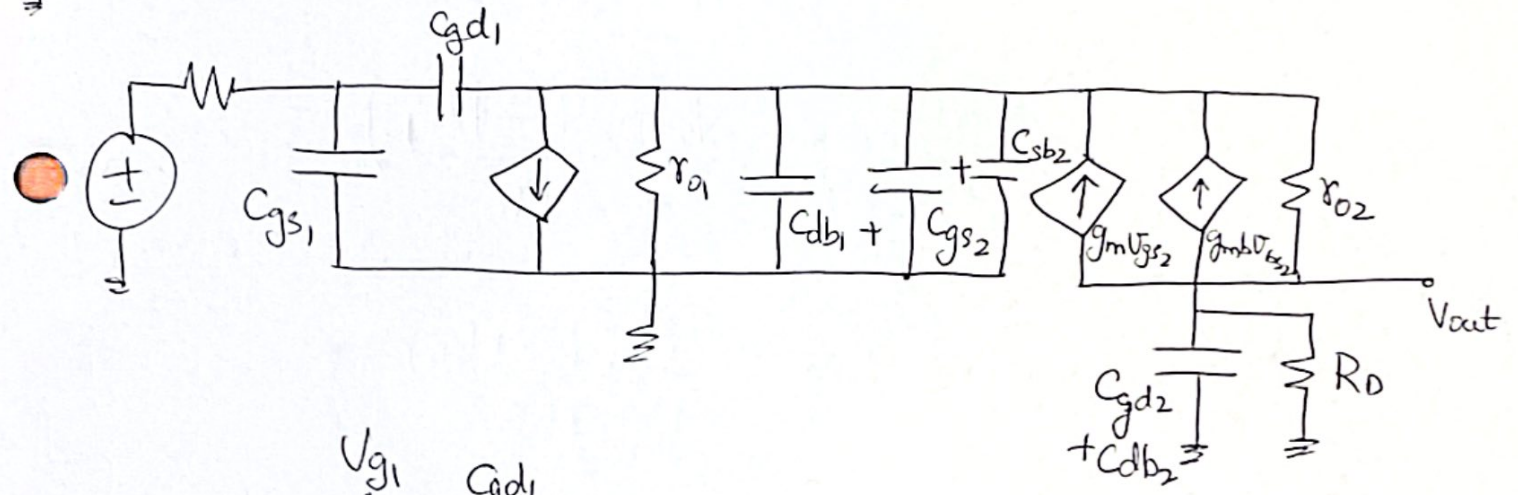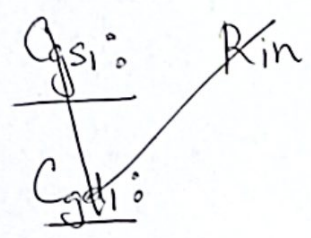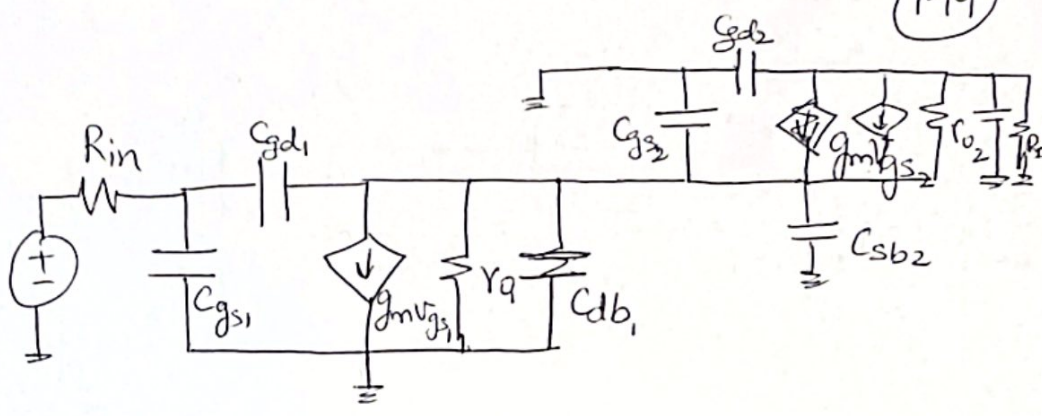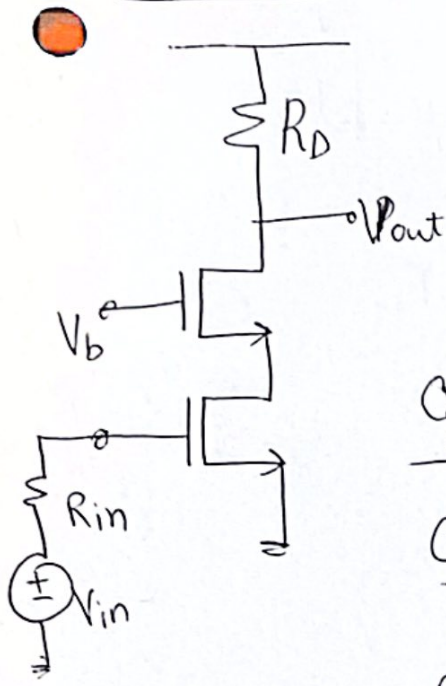

$$C_x = C_{db1} + C_{gs2} + C_{sb2}$$

$$C_y = C_{gd2} + C_{db2}$$

# OCTC

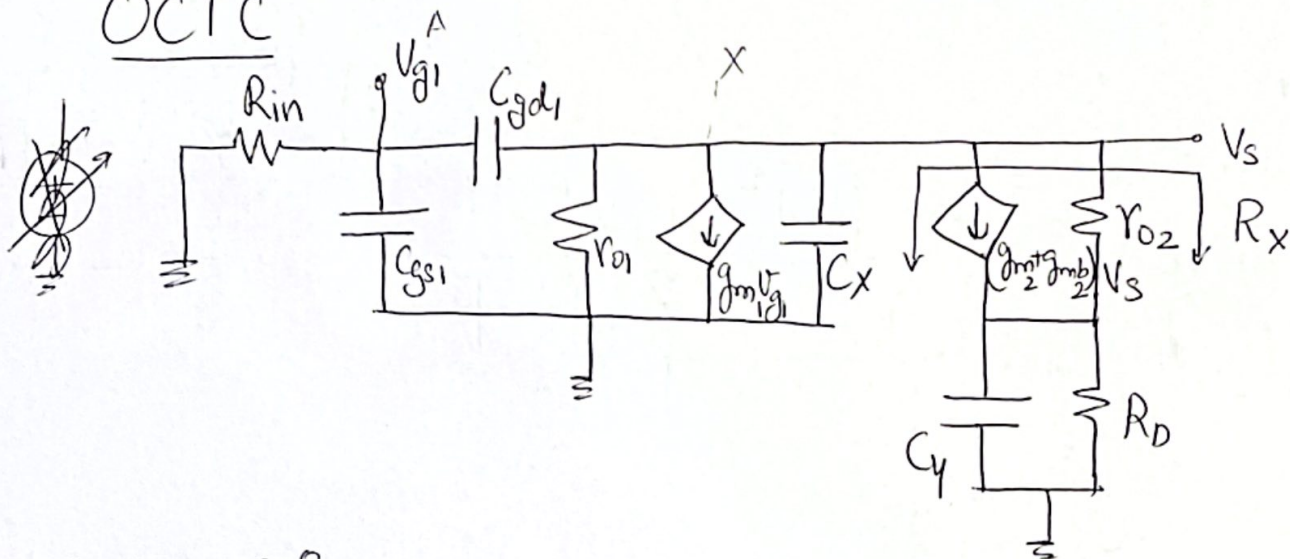

$C_{gs1} : R_{gs1}^o = R_{in}$

$C_{gd1} : R_x = \frac{V_x}{I_x} = \frac{V_x}{(g_{m2} + g_{mb2})V_x + \frac{(V_x - I_x R_D)}{r_{o2}}}$

$\Rightarrow V_x \left( (g_{m2} + g_{mb2}) r_{o2} + 1 \right) = I_x (r_{o2} + R_D)$

$\Rightarrow R_x = \frac{r_{o2} + R_D}{(g_{m2} + g_{mb2}) r_{o2} + 1} \approx \frac{1}{g_{m2} + g_{mb2}}$


Combining with  $r_{o1} \Rightarrow R_{gd1}^o = g_{m1} R_{in} R_x' + R_{in} + R_x'$

Where  $R_x' = R_x \parallel r_{o1}$

$\Rightarrow R_{gd1}^o = \frac{g_{m1} R_{in}}{g_{m2}} + R_{in} + \frac{1}{g_{m2}} \cong 2 R_{in}$   
 ↳ Dropped from  $g_m R_D$  to 2!

C<sub>x</sub>  
~~Req~~:  $Y_{01} \parallel R_x = R_x' = \frac{1}{g_{m2} + g_{mb2}}$

C<sub>y</sub>:

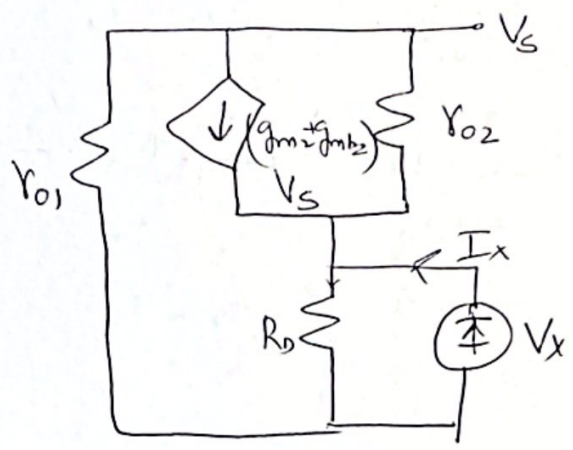

$$I_x - \frac{V_x}{R_D} = -(g_{m2} + g_{mb2})V_s + \frac{(V_x - V_s)}{Y_{02}}$$

$$V_s = \left( I_x - \frac{V_x}{R_D} \right) Y_{01}$$

$$\Rightarrow I_x - \frac{V_x}{R_D} = -(g_{m2} + g_{mb2}) \left( I_x - \frac{V_x}{R_D} \right) Y_{01} + \frac{V_x}{Y_{02}} - \left( I_x - \frac{V_x}{R_D} \right) \frac{Y_{01}}{Y_{02}}$$

$$\Rightarrow I_x \left( 1 + (g_{m2} + g_{mb2}) Y_{01} + \frac{Y_{01}}{Y_{02}} \right) = V_x \left( \frac{1}{R_D} + \frac{Y_{01}}{R_D} (g_{m2} + g_{mb2}) + \frac{1}{Y_{02}} + \frac{Y_{01}}{R_D Y_{02}} \right)$$

$$\Rightarrow R_x = \frac{1 + \frac{Y_{01}}{Y_{02}} + (g_{m2} + g_{mb2}) Y_{01}}{\left( \frac{1}{R_D} + \frac{Y_{01}}{R_D} (g_{m2} + g_{mb2}) + \frac{1}{Y_{02}} + \frac{Y_{01}}{R_D Y_{02}} \right)} \approx \frac{g_{m2} Y_{01}}{R_D} \approx R_D$$


$$\omega_{2dB} = \frac{1}{R_{in} C_{gs1} + \left[ R_{in} \left( 1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) + \frac{1}{g_{m2} + g_{mb2}} \right] C_{gd1} + \frac{(C_{db1} + C_{gs2} + C_{sb2})}{g_{m2} + g_{mb2}} + R_D (C_{gd2} + C_{db2})}$$

$$\approx \frac{1}{C_{gs1} R_{in} + \left( 2 R_{in} + \frac{1}{g_{m2}} \right) C_{gd1} + \frac{C_{gs2}}{g_{m2}} + C_{gd2} R_D}$$


↑  
only 2 instead of Miller!

→ Wide band.

Doing this by inspection!

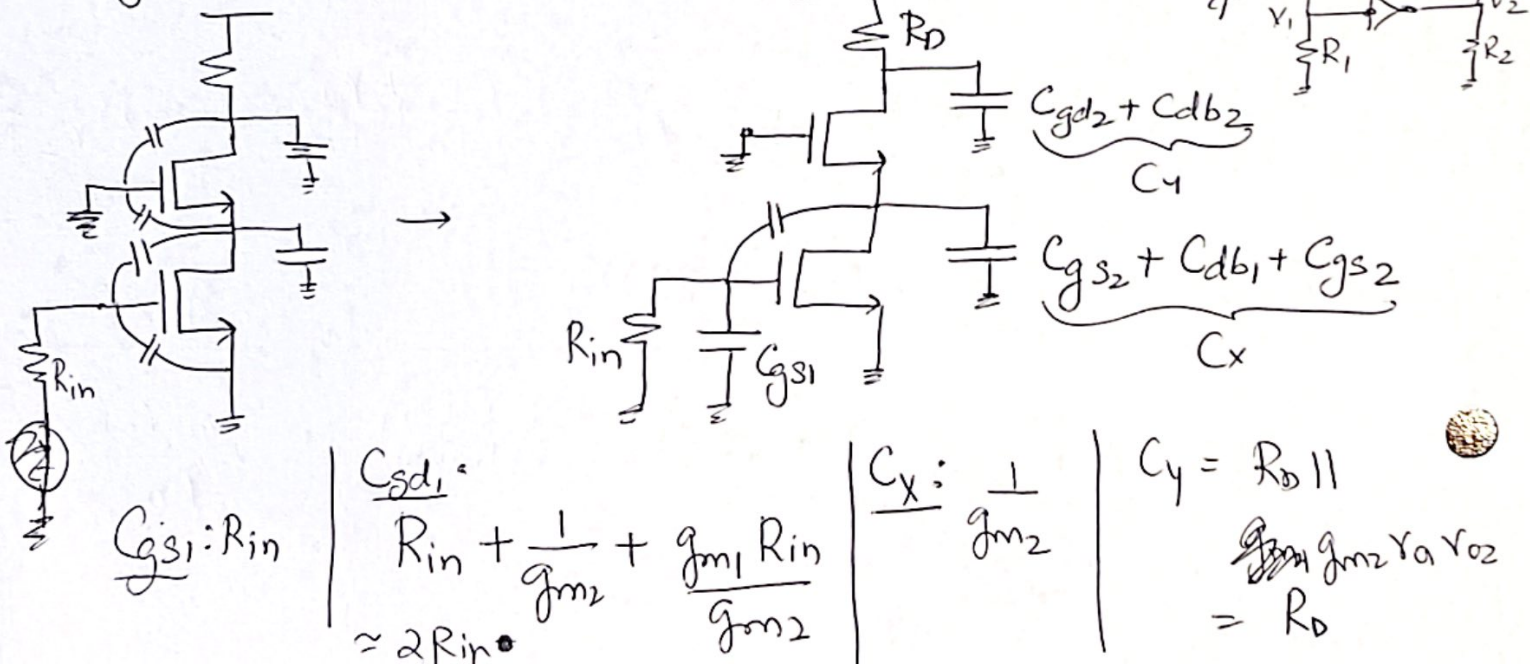

# Useful Trick

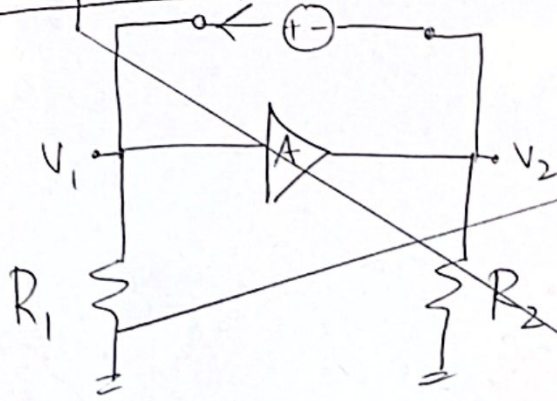


$$v_2 = A v_1$$

$$i_x = \frac{v_1}{R_1} = -\frac{v_2}{R_2}$$

$$v_x = v_1 - v_2$$

$$= i_x R_1$$

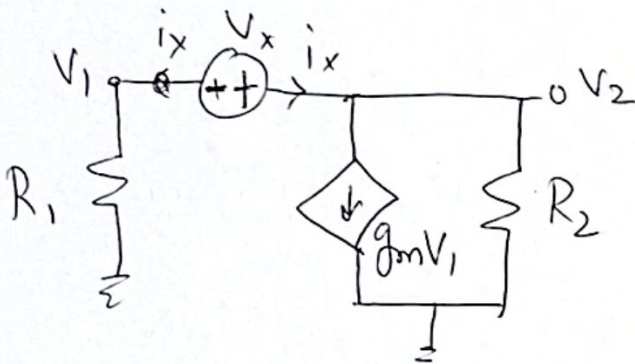

$$i_x = g_m v_1 + \frac{v_2}{R_2}$$

$$v_2 - v_1 = v_x$$

$$\frac{v_1}{R_1} = -i_x$$

$$\Rightarrow \left. \begin{array}{l} v_2 = v_x + \frac{-i_x R_1}{R_2} \\ v_1 = -i_x R_1 \end{array} \right\} \Rightarrow i_x = g_m (-i_x R_1) + \frac{v_x - i_x R_1}{R_2}$$

$$\Rightarrow i_x \left( 1 + g_m R_1 + \frac{R_1}{R_2} \right) = \frac{v_x}{R_2}$$

$$\Rightarrow \boxed{R_x = R_1 + R_2 + g_m R_1 R_2}$$